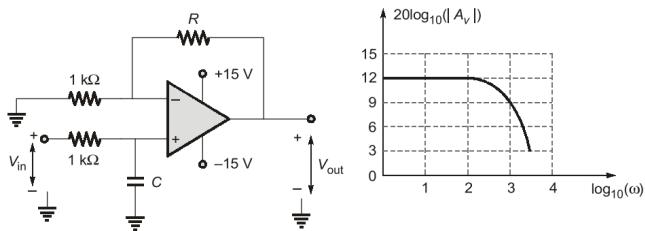


GATE 2022 EC

EE:1205 Signals and System
Indian Institute of Technology, Hyderabad

Prashant Maurya
EE23BTECH11218

Question 42: A circuit with an ideal OPAMP is shown. The Bode plot for the magnitude (in dB) of the gain transfer function $(A(j\omega)) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$ of the circuit is also provided (here, ω is the angular frequency in rad/s). The values of R and C are



- (A) $R = 3\text{ k}\Omega$, $C = 1\mu\text{F}$
- (B) $R = 1\text{ k}\Omega$, $C = 3\mu\text{F}$
- (C) $R = 4\text{ k}\Omega$, $C = 1\mu\text{F}$
- (D) $R = 3\text{ k}\Omega$, $C = 2\mu\text{F}$

Solution