

# GATE 2022 EC

EE:1205 Signals and System  
Indian Institute of Technology, Hyderabad

Prashant Maurya  
EE23BTECH11218

**Question 42:** A circuit with an ideal OPAMP is shown. The Bode plot for the magnitude (in dB) of the gain transfer function  $(A(j\omega)) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)}$  of the circuit is also provided (here,  $\omega$  is the angular frequency in  $rad/s$ ). The values of  $R$  and  $C$  are

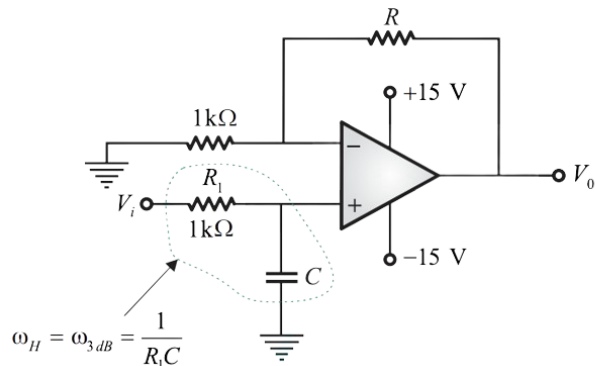
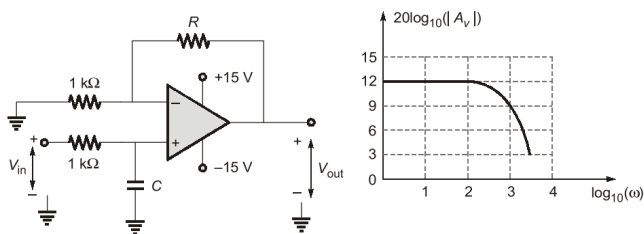


Fig. 1: Active Low Pass Filter

The given Op-Amp is first order active low pass filter, so low frequency ( $\omega = 0$ ) gain of given low-pass filter is,

- (A)  $R = 3k\Omega$ ,  $C = 1\mu F$
- (B)  $R = 1k\Omega$ ,  $C = 3\mu F$
- (C)  $R = 4k\Omega$ ,  $C = 1\mu F$
- (D)  $R = 3k\Omega$ ,  $C = 2\mu F$

**Solution**

Parameter	Description	Value
$R$	Resistance	?
$C$	Capacitance	?
$\omega_{dB}$	Cut-off frequency	1000
$A_V$	Gain Transfer	$\frac{V_{out}}{V_{in}}$

TABLE 1: Given Parameters

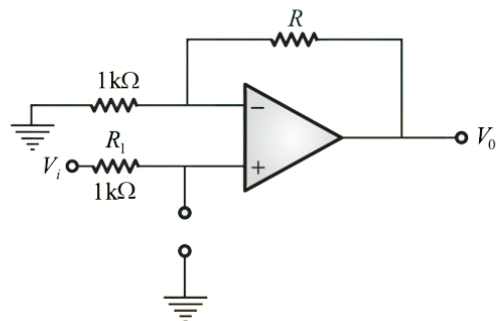


Fig. 2: Non-Inverting

The above OP-Amp circuit becomes as non-inverting closed loop Op-Amp, so gain ( $A_V$ ) is,

$$A_V = \left[ 1 + \frac{R}{1} \right] \quad (1)$$

$$= 1 + R \quad (2)$$

The 3-dB cut-off frequency of given low pass filter

circuit is,

$$\omega_{3dB} = \frac{R_1}{C} \text{ rad/s} \quad (3)$$

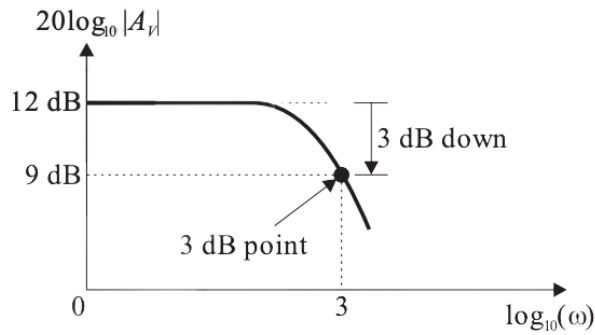


Fig. 3: bode magnitude plot

Low frequency ( $\omega = 0$ ) gain from bode magnitude plot is,

$$\Rightarrow 12 \text{ dB} = 20 \log_{10} (A_v) \quad (4)$$

$$A_v = \text{Antilog} \left[ \frac{12}{20} \right] \quad (5)$$

$$\Rightarrow 1 + R = 4 \quad (6)$$

$$R = 3k\Omega \quad (7)$$

The 3-dB frequency from bode magnitude plot,

$$\Rightarrow \log_{10} \omega_{3dB} = 3 \quad (8)$$

$$\omega_{3dB} = 1000 \text{ rad/sec} \quad (9)$$

$$\omega_{3dB} = \frac{1}{R_1 C} \quad (10)$$

$$= 1000 \quad (11)$$

$$\Rightarrow C = \frac{1}{1000 R_1} \quad (12)$$

$$= 1 \mu F \quad (13)$$

Hence, the correct option is (A).